

**Exercise 1.** Find the sum of following pairs of hex numbers


- a. 3E91 + 2F93
- b. 91B + 6F2
- c. ABC + BEF
- d. 2FFE + 0002

**Exercise 2.** Perform the following subtractions on the pairs of hex numbers

- a. 3E91 – 2F93
- b. 91B – 6F2
- c. 0300 - 005A
- d. 0200 – 0003

**Exercise 3.** Design a 2 bit Full adder using basic gates (AND, OR, NOT)


**Exercise 4.**

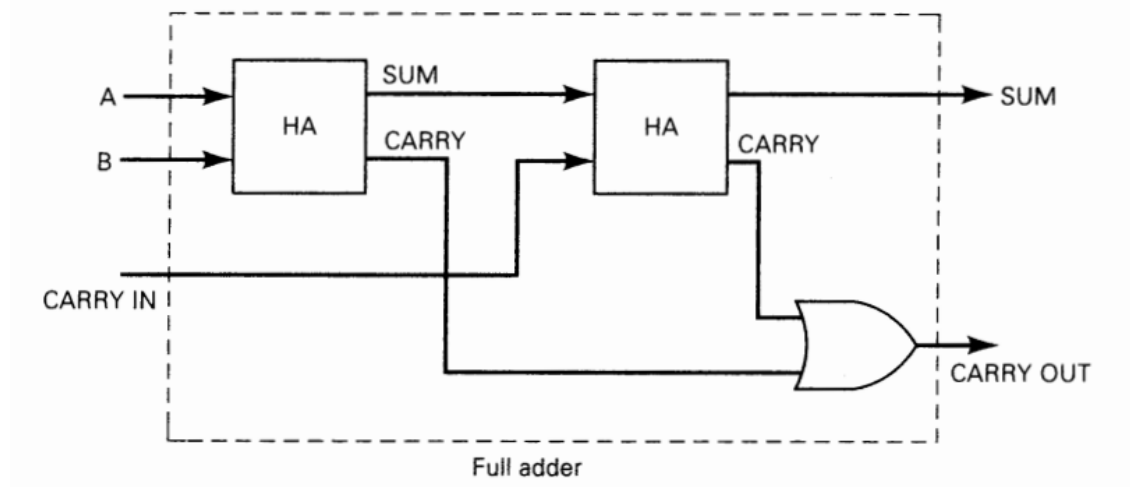

**Figure 1. Full adder**

A Full-adder can be implemented in many different ways. Figure 1 shows how one may be constructed from two half adder. Construct the truth table for this arrangement, and verify that it operates as a Full-adder

**Exercise 5.**

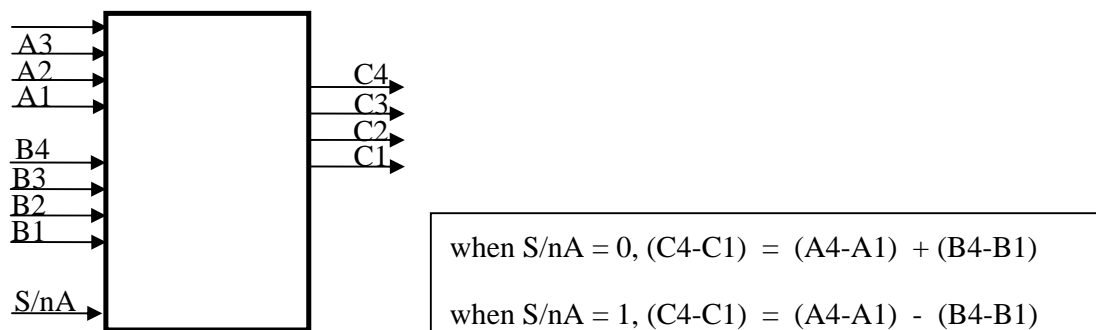

**Figure 2. Adder/subtractor circuit**

Using 74LS283 (adder IC) and 74LS86 (Xor gate) to design a Adder/Subtractor circuit in Figure 2.