

Chapter 6: Multilevel Combinational Circuits

Name: Lương Văn Minh

No. : 09070452

Overview

- 6.1 Boolean Networks
- 6.2 Special Classes of Circuits
- 6.3 Binary Decision Diagrams

Overview



- 6.1 Boolean Networks
- 6.2 Special Classes of Circuits
- 6.3 Binary Decision Diagrams

6.1 Boolean Networks

- A combinational logic circuit is represented as a labeled, directed, acyclic graph (DAG) $G = (V, E)$.
- Each vertex v is labeled with the name of a primitive gate such as AND, OR, or NOT, or with the name of a primary input or output.
- Each gate and edge in the circuit has an associated delay.

  6.1 Boolean Networks (cont.)

- Directed acyclic graph (DAG) $G = (V, E)$
example:




6.1 Boolean Networks (cont.)

- The fan-out of a gate g (or a wire) is defined as the set of gates that use as an input the value generated by g .
- A Boolean network η is a DAG, each node i in η there is an associated cover F_i and a Boolean variable y_i representing the output of F_i .
- May implement a Boolean network η by replacing each cover F_i in η by a NAND-NAND network.

6.1 Boolean Networks (cont.)

- Boolean Networks example:

	f_1	f_2	f_3	f_4	f_5
0	0	0	0	0	0
1	1	1	1	0	0
1	1	1	1	0	0
1	0	0	1	0	0
0	0	1	0	0	0
1	1	1	1	1	0
1	1	0	1	1	0
1	1	1	1	1	1
j_1	5	3	3	3	5
j_2	2	5	1	4	4
j_3	4	4	5	4	1

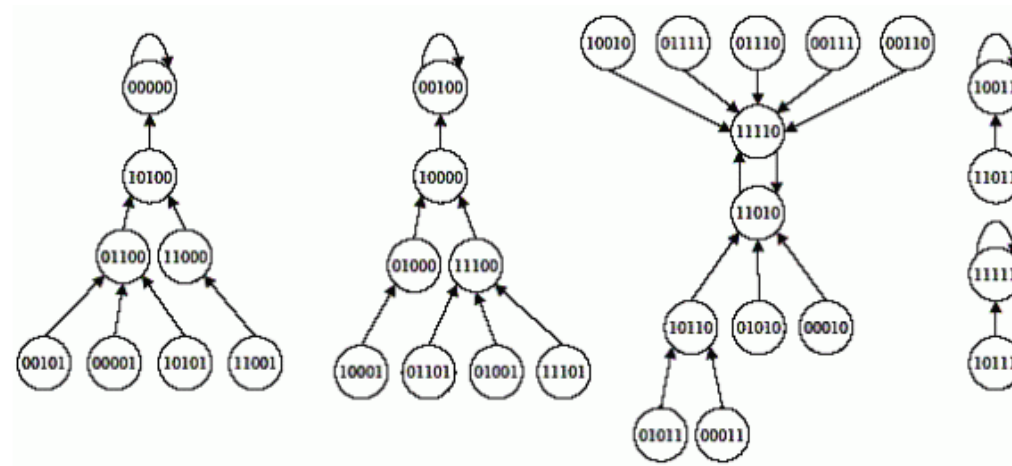

Overview

- 6.1 Boolean Networks
- 6.2 Special Classes of Circuits
- 6.3 Binary Decision Diagrams

6.2 Special Classes of Circuits

- 6.2.1 Fan-out-Free Circuits
- 6.2.2 Leaf-DAG Circuits
- 6.2.3 Algebraically Factored Circuits
- 6.2.4 Multiplexor-Based Circuits

6.2.1 Fan-out-Free Circuits

- A fan-out-free circuit is one in which the output of each gate and each circuit input is connected to at most one gate.
- A fan-out-free circuit is also called a tree. For example, the circuit $f = a b + c d$ is a tree.

6.2.1 Fan-out-Free Circuits (cont.)

- Many testability results have been proven.

These are:

1. There exists a set of tests which detect all single and multiple stuck-at fault and is of minimal cardinality among all test sets for single faults.
2. The number of tests required to detect all stuck-at faults is bounded above by $n:1$ and is bounded below by $2\sqrt{n}$ where n is the number of circuit inputs.
3. A set of tests which detect all stuck-at faults on circuit inputs will detect all single stuck-at faults

6.2.2 Leaf-DAG Circuits

- A leaf-DAG circuit is a generalization of a fan-out-tree circuit where only the primary inputs are allowed to fan out to multiple gates.
- Any circuit can be converted into a leaf-DAG circuit by gate duplication.

6.2.3 Algebraically Factored Circuits

- An algebraically factored circuit is a circuit which is derived by a sequence of algebraic transformations from a two-level sum-of-products representation.
- For example, the circuit $(a + b) \cdot (c + d)$ is an algebraic factorization of the sum-of-products expression $a.c + a.d + b.c + b.d$

6.2.4 Multiplexor-Based Circuits

- Arbitrary Boolean function can be implemented using circuits whose only constituent gates are two-input multiplexors.

Overview



- 6.1 Boolean Networks
- 6.2 Special Classes of Circuits
- 6.3 Binary Decision Diagrams

6.3 Binary Decision Diagrams

- Binary decision diagrams (BDDs) were first proposed by Lee, further developed by Akers
- BDD is a rooted, directed graph with vertex set V containing two types of vertices:
 1. a nonterminal vertex v has as attributes an argument index $\text{index}(v) \in \{1, \dots, n\}$ and two children $\text{low}(v), \text{high}(v)$.
 2. a terminal vertex v has as an attribute a value $\text{value}(v) \in \{0, 1\}$

6.3 Binary Decision Diagrams (cont.)

BDDs example:

 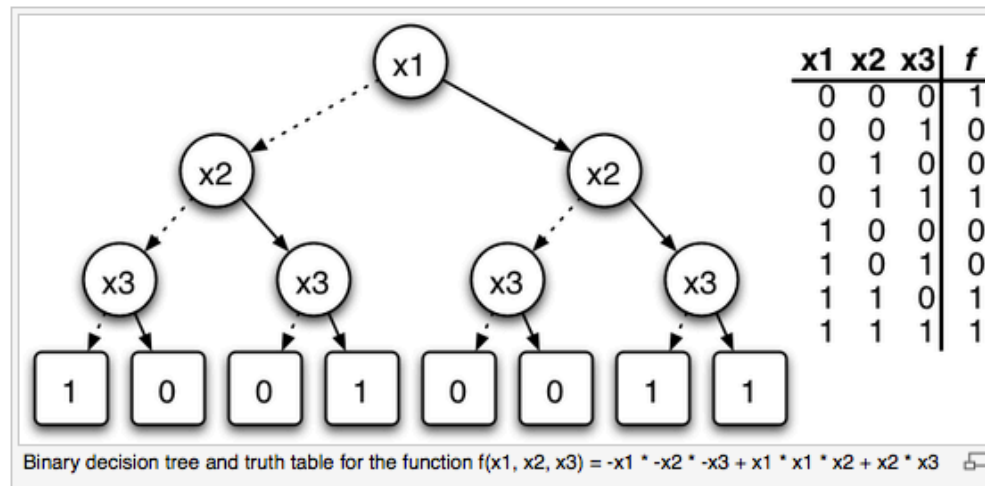

6.3 Binary Decision Diagrams (cont.)

- A BDD G having root vertex v defines a function f_v defined recursively as:
 1. If v is a terminal vertex:
 - a) If $\text{value}(v) = 1$ then $f_v = 1$
 - b) If $\text{value}(v) = 0$ then $f_v = 0$
 2. If v is a nonterminal vertex with $\text{index}(v) = i$ then f_v is the function:
$$f_v(x_1, \dots, x_n) = \neg x_i \cdot f_{\text{low}(v)}(x_1, \dots, x_n) + x_i \cdot f_{\text{high}(v)}(x_1, \dots, x_n)$$
 x_i called the decision variable for vertex v

6.3 Binary Decision Diagrams (cont.)

- BDDs can be categorized based on two additional properties:
 1. Freedom: When traversing any path from a terminal vertex to the root vertex we encounter each decision variable at most one
 2. Ordered: place the restriction that for any nonterminal vertex v .
 - if $\text{low}(v)$ is also nonterminal then must have $\text{index}(v) < \text{index}(\text{low}(v))$
 - if $\text{high}(v)$ is also nonterminal then must have $\text{index}(v) < \text{index}(\text{high}(v))$