

# MULTI-LEVEL LOGIC OPTIMIZATION(CONT)

Nguyễn Phạm Anh Khoa  
Trần Huy Vũ

## CONTENT

- Boolean division
- Don't care based optimization

## BOOLEAN DIVISION

- Algebraic division:
- Example:  $f = abd + cd + abe + ace$ , assumed  $g = ab + c$   
 $= d(ab + c) + abe + ace$
- More optimal:  $f = (ab + c)(ae + d)$
- Why?
- Algebraic division:  $f = h.g + r$
- $h$  and  $g$  are orthogonal

## BOOLEAN DIVISION

- Boolean division:  $f = h.g + r$
- $h$  and  $g$  can share:
- A common literal  $x$   
 $a + bc = (a + b).(a + c)$
- Literal  $x$  and  $x'$   
 $ab + a'c + bc = (a + b)(a' + c)$

## BOOLEAN DIVISION

- Provided  $f, g$ ; reexpress  $f = h.g + r$  (minimized)
- Label  $g$  as an input  $G$
- Construct a function  $F = \begin{cases} \text{Don't care, } G \neq g \\ f, G = g \end{cases}$
- DC set of  $F = G \wedge g' = G.g' + G'.g$
- ON set of  $F = f \cdot (G.g + G'.g') = f \cdot (G.g' + G'.g)'$
- Apply some known optimization algorithm on  $F$
- Note:  $F \equiv f$ , because  $G = g$



## DON'T CARE BASED OPTIMIZATION


Two types of Don't Care conditions:

- ❖ External Don't Cares: defined by user, example: the DC-set
- ❖ Internal Don't Cares: exist because of the structure of the boolean network. Two types of Internal Don't Cares:
  - Satisfiability don't care
  - Observability don't care


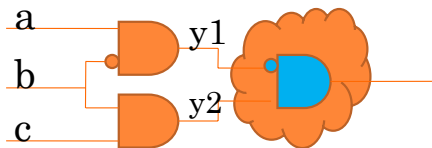
## SATISFIABILITY DON'T CARES

If input cannot occur, don't care the output




y1	y2	f	y1	y2	f
0	0	0	0	0	0
0	1	1	0	1	1
1	0	0	1	0	0
1	1	0	1	1	x

$f = y2$   
 Never occur



## SATISFIABILITY DON'T CARES

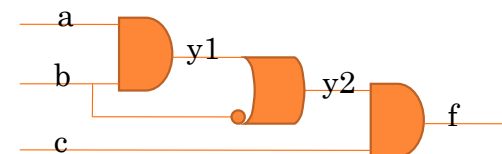

- $Y_j = F_j(x, y)$
- Example:  $Y_2 = \text{OR}(\sim b, Y_1)$
- Which configuration of inputs of  $Y_2$  cannot occur?


Answer:  $Y_1.F1' + Y_1'.F1$

$Y_1.(a' + b') + Y_1'.a.b$

Example:  $Y_1 = 1, b = 0$  cannot occur




## SATISFIABILITY DON'T CARE

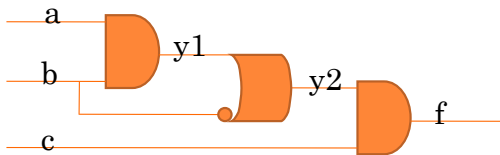

- Satisfiability Don't Care Set:
- $SDC = \sum_j (Y_j \cdot F_j' + Y_j' \cdot F_j)$
- Optimize a node **N**:
- Use Satisfiability Don't Care Set of Nodes that fan-out to **N**



## OBSERVABILITY DON'T CARES

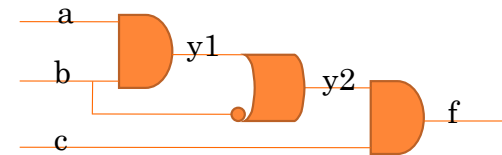

- Says: The output **F** can observe the input **X** (**X** can be observed at output **F**) if changes of **X** make **F** changed
- Example: if  $c = 1$  then  $y2$  can be observed at **F**  
if  $c = 0$  then  $y2$  cannot be observed at **F**




## OBSERVABILITY DON'T CARES

- Define Observability of node  $Y_j$ :
- $\partial F_k / \partial Y_j = F_{kY_j} \text{ XOR } F_{k\bar{Y}_j}$  (Boolean difference)
- $\partial F_k / \partial Y_j = 0$  (or  $F_{kY_j} = F_{k\bar{Y}_j}$ ) :  $Y_j$  cannot be observed at **F**
- $F_{kY_j} = F_{k\bar{Y}_j}$  : Observability Don't Care condition for  $Y_j$
- Observability Don't Care Set of node  $Y_j$
- $ODC = \prod_{\text{all outputs } k} (F_{kY_j} = F_{k\bar{Y}_j}) = \prod_{\text{all output } k} (\partial F_k / \partial Y_j)'$



## DON'T-CARE GENERATION

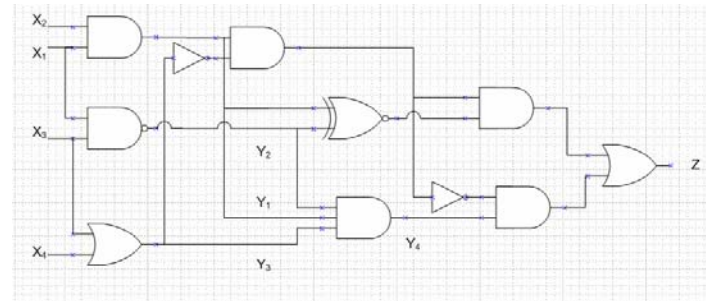

$$Y_1 = x_1 \cdot x_2$$

$$Y_2 = x_1 \cdot x_3$$

$$Y_3 = x_3 + x_4$$

$$Y_3=0 \rightarrow Y_2=1$$

000



100

## DON'T-CARE GENERATION

Local satisfiability don't-care set for node 4

$$SDC_4 = \overline{y_2} \cdot \overline{y_3}$$

Sum of product representation for node 4

$$F_4 = y_1 \cdot y_2 \cdot y_3$$

13

## DON'T-CARE GENERATION

The function at the primary output Z

$$Z = \overline{x_1} \cdot \overline{x_2} \cdot \overline{x_3} \cdot \overline{x_4} \cdot y_4 + \overline{x_1} \oplus x_2 \cdot x_1 \cdot x_2 \cdot \overline{x_3} \cdot \overline{x_4}$$

→  $Z = (\overline{x_1} + \overline{x_2} + x_3 + x_4) y_4 + x_1 \cdot x_2 \cdot \overline{x_3} \cdot \overline{x_4}$

→ Cofactor of z with respect to  $y_4$  are

$$Z_{y_4} = \overline{x_1} + \overline{x_2} + x_3 + x_4 + x_1 \cdot x_2 \cdot \overline{x_3} \cdot \overline{x_4} = 1$$

$$Z_{\overline{y_4}} = x_1 \cdot x_2 \cdot \overline{x_3} \cdot \overline{x_4}$$

14

## DON'T-CARE GENERATION

Finally,  $ODC_4$  can be expressed as

$$ODC_4 = \overline{z_{y_4}} \oplus z_{\overline{y_4}} = x_1 \cdot x_2 \cdot \overline{x_3} \cdot \overline{x_4}$$

→ **110** is not in the local care set

→  $SDC_4 \cup DC_4 = \overline{y_2} \cdot \overline{y_3} + y_1 \cdot y_2 \cdot \overline{y_3}$

→  $F_4 = y_1 \cdot y_2$

15

## DON'T-CARE GENERATION

1. Select a node  $i$  in the Boolean network
2. For each primary output  $z_k$ , compute cofactor  $z_k$  respect to  $y_i$  and  $\overline{y_i}$
3. Compute

$$C_i = \sum_{\text{All outputs } k} z_{y_i} \oplus z_{\overline{y_i}}$$

4.  $C_i \rightarrow LC_i$
5. Minimize  $F_i$  with local care set  $SDC_i \cup ODC_i = \overline{LC_i}$

16

## RANGE COMPUTATION

Characteristic function

$$\text{Let } f: B^N \rightarrow B^M$$

Let  $A \subseteq B^N$ ,  $n_A: B^N \rightarrow \{0,1\}$  which is defined as  
 $n_A(x) = 1$  if  $x \in A$ , else  $n_A(x) = 0$

Smoothing function

$$\text{Let } f: B^N \rightarrow B \text{ and } x = (x_1, x_2, \dots, x_n)$$

$$\begin{aligned} S_x f &= S_{x_1} S_{x_2} \dots S_{x_n} f \\ S_{x_i} f &= f_{x_i} + f_{\bar{x}_i} \end{aligned}$$

17

## RANGE COMPUTATION

Transition relation

$$\text{Let } f: B^N \rightarrow B^M$$

$$\longrightarrow F: B^N \times B^M \rightarrow B$$

$$F(x,y) = 1 \iff (x,y) \in B^N \times B^M \text{ and } y = f(x)$$

$$\iff F(x,y) = \prod_{1 \leq i \leq M} (y_i \oplus \overline{f_i(x)})$$

$$\longrightarrow f(A) = \{y: \exists x (x \in A) \wedge F(x,y) = 1\}$$

$$\longrightarrow f(A)(y) = S_x (F(x,y) \cdot A(x))$$

18

## RANGE COMPUTATION

Example:

$$\begin{aligned} y_1 &= x_1 \cdot x_2 \\ y_2 &= \overline{x_1} + \overline{x_3} \\ y_3 &= x_3 + x_4 \end{aligned}$$

$$\longrightarrow F(x,y) = y_1 \oplus (x_1 \cdot x_2) \cdot y_2 \oplus (\overline{x_1} + \overline{x_3}) \cdot y_3 \oplus (x_3 + x_4)$$

$$C_4 = A(x) = \overline{x_1} + \overline{x_2} + x_3 + x_4$$

$$\longrightarrow LC_4 = f(A)(y) = S_x (F(x,y) \cdot A(x))$$

$$\longrightarrow \overline{LC}_4 = \overline{y_2} \cdot \overline{y_3} + y_1 \cdot y_2 \cdot \overline{y_3}$$

19